

Gebze Technical University

Computer Engineering

CSE 331

ASSIGNMENT 3 REPORT

ERSİN ALÇIN

1801042692

Making of ALU To achieve an ALU which can select an operation in a list of 8 I used 8x1 mux to select which operation to return. Before that I calculated all outcomes and directed them to 8x1 mux. ALU Modules (Explained) Mux To assemble a 8x1 mux I needed 2 4x1 mux and 1 2x1 mux. And to construct a 4x1 mux I needed 3 more 2x1 mux. So, I started this assignment by building a 2x1 mux in Verilog. After first successful 2x1 mux I needed 32 bit input and output version of this mux to create 32 bit 4x1 and 8x1 muxes. In the way I used 32 times 2x1 muxes. . Simple Gates After successful 1 bit and 32-bit 2x1 mux, I wrote 4x1 mux in bot 1 bit and 32 bits. After them finally wrote the 32-bit 8x1 mux to create 32-bit ALU.

Then I wrote simple Gates and full_adder_32, subtracter_32 .

```
module mux_2x1(out, in1, in2, select);
input in1, in2;
input select;
output out;
wire a,b, notSelect;

and first_select(a, in2, select);
not reverse_select(notSelect, select);
and second_select(b, notSelect, in1);
or out_select(out, a, b);

endmodule
```

```
module andGate(Y,A,B);
output [31:0] Y;
input [31:0] A;
input [31:0] B;

and and1(Y[0],A[0],B[0]);
and and2(Y[1],A[1],B[1]);
and and3(Y[2],A[2],B[2]);
and and4(Y[3],A[3],B[3]);
and and5(Y[4],A[4],B[4]);
and and55(Y[5],A[5],B[5]);
and and6(Y[6],A[6],B[6]);
and and7(Y[7],A[7],B[7]);
and and8(Y[8],A[8],B[8]);
and and9(Y[9],A[9],B[9]);
and and10(Y[10],A[10],B[10]);
and and11(Y[11],A[11],B[11]);
and and12(Y[12],A[12],B[12]);
and and14(Y[13],A[13],B[13]);
and and15(Y[14],A[14],B[14]);
and and16(Y[15],A[15],B[15]);
and and17(Y[16],A[16],B[16]);
and and18(Y[17],A[17],B[17]);
and and19(Y[18],A[18],B[18]);
and and20(Y[19],A[19],B[19]);
and and21(Y[20],A[20],B[20]);
and and22(Y[21],A[21],B[21]);
and and23(Y[22],A[22],B[22]);
and and24(Y[23],A[23],B[23]);
and and25(Y[24],A[24],B[24]);
and and26(Y[25],A[25],B[25]);
and and27(Y[26],A[26],B[26]);
and and28(Y[27],A[27],B[27]);
and and29(Y[28],A[28],B[28]);
```

```
module xorGate(Y,A,B);
```

```
output [31:0] Y;
```

```
input [31:0] A;
```

```
input [31:0] B;
```

```

xor xor1(Y[0],A[0],B[0]);
xor xor2(Y[1],A[1],B[1]);
xor xor3(Y[2],A[2],B[2]);
xor xor4(Y[3],A[3],B[3]);
xor xor5(Y[4],A[4],B[4]);
xor xor6(Y[5],A[5],B[5]);
xor xor7(Y[6],A[6],B[6]);
xor xor8(Y[7],A[7],B[7]);
xor xor9(Y[8],A[8],B[8]);
xor xor10(Y[9],A[9],B[9]);
xor xor11(Y[10],A[10],B[10]);
xor xor12(Y[11],A[11],B[11]);
xor xor13(Y[12],A[12],B[12]);
xor xor15(Y[13],A[13],B[13]);
xor xor16(Y[14],A[14],B[14]);
xor xor17(Y[15],A[15],B[15]);
xor xor18(Y[16],A[16],B[16]);
xor xor19(Y[17],A[17],B[17]);
xor xor20(Y[18],A[18],B[18]);
xor xor21(Y[19],A[19],B[19]);
xor xor22(Y[20],A[20],B[20]);
xor xor23(Y[21],A[21],B[21]);
xor xor24(Y[22],A[22],B[22]);
xor xor25(Y[23],A[23],B[23]);
xor xor26(Y[24],A[24],B[24]);
xor xor27(Y[25],A[25],B[25]);
xor xor28(Y[26],A[26],B[26]);

```

```
module full_adder_32 (out, carry_out, in1, in2, carry_in);
```

```
input [31:0] in1, in2;
```

```
input carry_in;
```

```
output carry_out;
```

```
output [31:0] out;
```

```
wire [30:0] carry;
```

```

full_adder FA1(out[0], carry[0], in1[0], in2[0], carry_in),
FA2(out[1], carry[1], in1[1], in2[1], carry[0]),
FA3(out[2], carry[2], in1[2], in2[2], carry[1]),
FA4(out[3], carry[3], in1[3], in2[3], carry[2]),
FA5(out[4], carry[4], in1[4], in2[4], carry[3]),
FA6(out[5], carry[5], in1[5], in2[5], carry[4]),
FA7(out[6], carry[6], in1[6], in2[6], carry[5]),
FA8(out[7], carry[7], in1[7], in2[7], carry[6]),
FA9(out[8], carry[8], in1[8], in2[8], carry[7]),
FA10(out[9], carry[9], in1[9], in2[9], carry[8]),
FA11(out[10], carry[10], in1[10], in2[10], carry[9]),
FA12(out[11], carry[11], in1[11], in2[11], carry[10]),
FA13(out[12], carry[12], in1[12], in2[12], carry[11]),
FA14(out[13], carry[13], in1[13], in2[13], carry[12]),
FA15(out[14], carry[14], in1[14], in2[14], carry[13]),
FA16(out[15], carry[15], in1[15], in2[15], carry[14]),
FA17(out[16], carry[16], in1[16], in2[16], carry[15]),
FA18(out[17], carry[17], in1[17], in2[17], carry[16]),
FA19(out[18], carry[18], in1[18], in2[18], carry[17]),
FA20(out[19], carry[19], in1[19], in2[19], carry[18]),
FA21(out[20], carry[20], in1[20], in2[20], carry[19]),
FA22(out[21], carry[21], in1[21], in2[21], carry[20]),
FA23(out[22], carry[22], in1[22], in2[22], carry[21]),
FA24(out[23], carry[23], in1[23], in2[23], carry[22]),
FA25(out[24], carry[24], in1[24], in2[24], carry[23]),
FA26(out[25], carry[25], in1[25], in2[25], carry[24]),

```

```
module subtracter_32 (out, in1, in2);
```

```
input [31:0] in1, in2;
```

```
output [31:0] out;
```

```
wire [31:0] a;
```

```
wire carry;
```


```
notGate NOT(a, in2);
```

```
full_adder_32 FA(out, carry, in1, a, 32'b1);
```

```
endmodule
```

Schematic Design

ALU

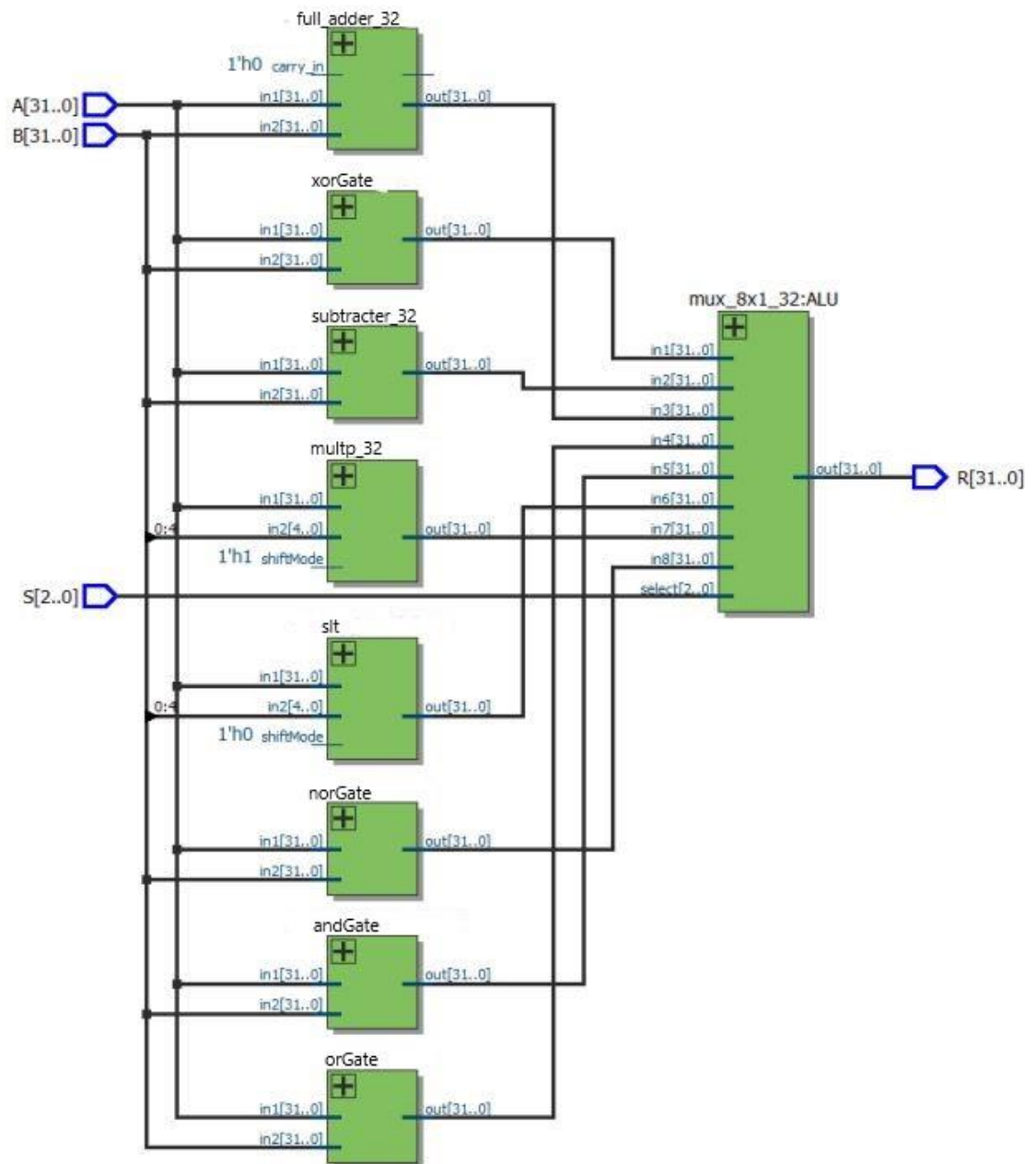

ModelSim Results

